LAB 4 ALU

Design a circuit with the following.

- Four 8-bit registers
- One 8-bit input port
- One 8-bit output port
- extra 1-bit sign output
- One 8-bit unidirectional tribus
- One arithmetic logic unit with two 8-bit input ports and one 8-bit output port. That makes operations on next slide.
- Necessary MUX components in order to make a generic purpose datapath with ALU.

Following operations are supported (X,Y,Z are three registers):

- input X,inputvalue: Input value is transferred to X from the input port.
- output X: Content of X is transferred to the output port in signed format with sign bit.
- outputu X: Content of X is transferred to the output port in unsigned format.

ALU OPERATIONS

- add Z, X, Y: Contents of X and Y are added and the result is transferred to Z.
- mul Z, X, Y: Contents of X and Y are multiplied and the result is transferred to Z.
- sub Z, X, Y: Content of Y is subtracted from content of X and the result is transferred to Z.
- div Z, X, Y: Content of Y is divided from content of X and the result is transferred to Z.
- shl Z, X: Content of X is shifted 1 bit left and the result is transferred to Z.
- shr Z, X: Content of X is shifted 1 bit right and the result is transferred to Z.
- and Z, X, Y: Contents of X and Y are bitwise-anded and the result is transferred to Z.
- or Z, X, Y: Contents of X and Y are bitwise-ored and the result is transferred to Z.

Two's complement

Three-bit signed integers


Decimal *	Binary (two's-complement * representation)	Two's complement \$ (23 - n)2
0	000	000
1	001	111
2	010	110
3	011	101
-4	100	100
-3	101	011
-2	110	010
-1	111	001

Eight-bit signed integers

Decimal *	Binary (two's-complement * representation)	Two's complement \$ (2 ^s - n) ₂
0	0000 0000	0000 0000
1	0000 0001	1111 1111
2	0000 0010	1111 1110
126	0111 1110	1000 0010
127	0111 1111	1000 0001
-128	1000 0000	1000 0000
-127	1000 0001	0111 1111
-126	1000 0010	0111 1110
-2	1111 1110	0000 0010
-1	1111 1111	0000 0001

Adding Unsigned Numbers

	Unsigned Binary
1 (carry)	110 (carry)
06	0110
+07	+0111
13	1101

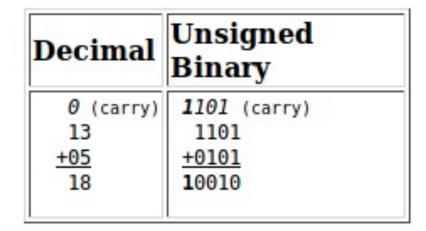

Adding Signed Numbers

Decimal	Signed Binary
-2 <u>+3</u> 1	1110 (carry) 1110 +0011 0001
Decimal	Signed Binary
-5 <u>+3</u> -2	011 (carry) 1011 +0011 1110
Decimal	Signed Binary
-4 -3 -7	1100 (carry) 1100 +1101 1001

Decimal	Signed Binary
6 <u>+3</u> 9	110 (carry) 0110 +0011 1001
Decimal Signed Binary	
-7 <u>-3</u> -10	1001 (carry) 1001 +1101 0110

Subtract Signed Numbers

Decimal	Signed Binary
5 3 2	0101 1101 + - - - -

Decimal	Signed Binary
3	0011
- 5	+ 1011
- 2	1110

Example 1

input r1,74

input r2,42

sub r3,r1,r2

out r3

input r4,-45

add r4,r4,r3

out r4

outu r4

Example 2

input r3,116 input r2,12

div r4,r3,r2

out r4

input r1,-7

mul r1,r1,r4

out r1

outu r1

Example 3

input r1,34

input r2,110

and r3,r1,r2

out r3

input r4,-45

or r4,r4,r3


out r4

outu r4

Example 4

input r3,26 input r2,120 shr r2,r2 shl r1,r1 out r1 input r3,-7 add r4,r1,r2 sub r3,r3,r4 out r3 outu r3


Sample scf file for Example 1

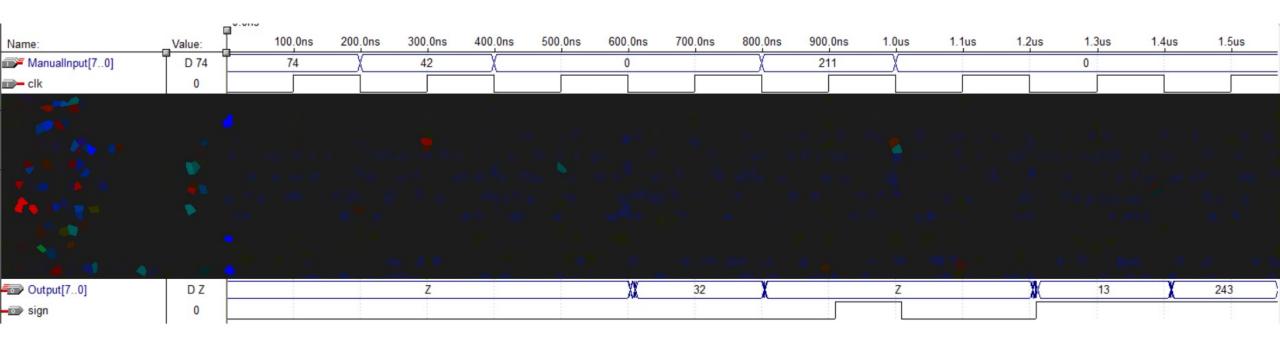

Hint 1

You can create your ALU as a symbol file and include it to your main project with: File-> Create Default Symbol.

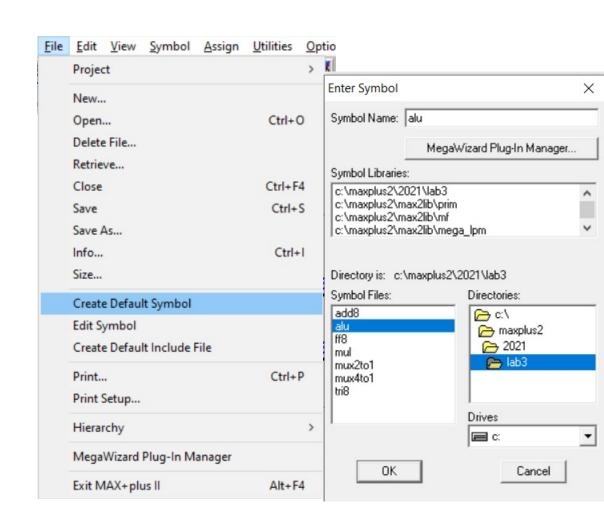After than you can add it with Right Click to Plane -> Enter Symbol -> your Component



*Note:If you change your symbol file you have to recreate default symbol and delete previous component to get changes.