

LAB 3

Datapath

LABWORK

Design a circuit with:

4 of 8 bit Register (Flipflop)

1 of 8 bit adder

3 of 8 bit 4 optional MUX

4 of 8 bit 2 optional MUX

1 of 8 bit Unidirectional Tri-BUS

and necessary controller signals and inputs/outputs to do add operation.

Timeline:

T: load data to Register A (A0 Hex)

T+1: load data to Register B (0B Hex)

T+2: add the data in register A and register B to Register C

T+3: Show output of register C

T+4: load data to Register D (06Hex)

T+5: add the data in register C and register D to register C


T+6: Show output of register D

T+7: Show output of register C

T+8: Show output of register B

T+9: Show output of register A

Example output

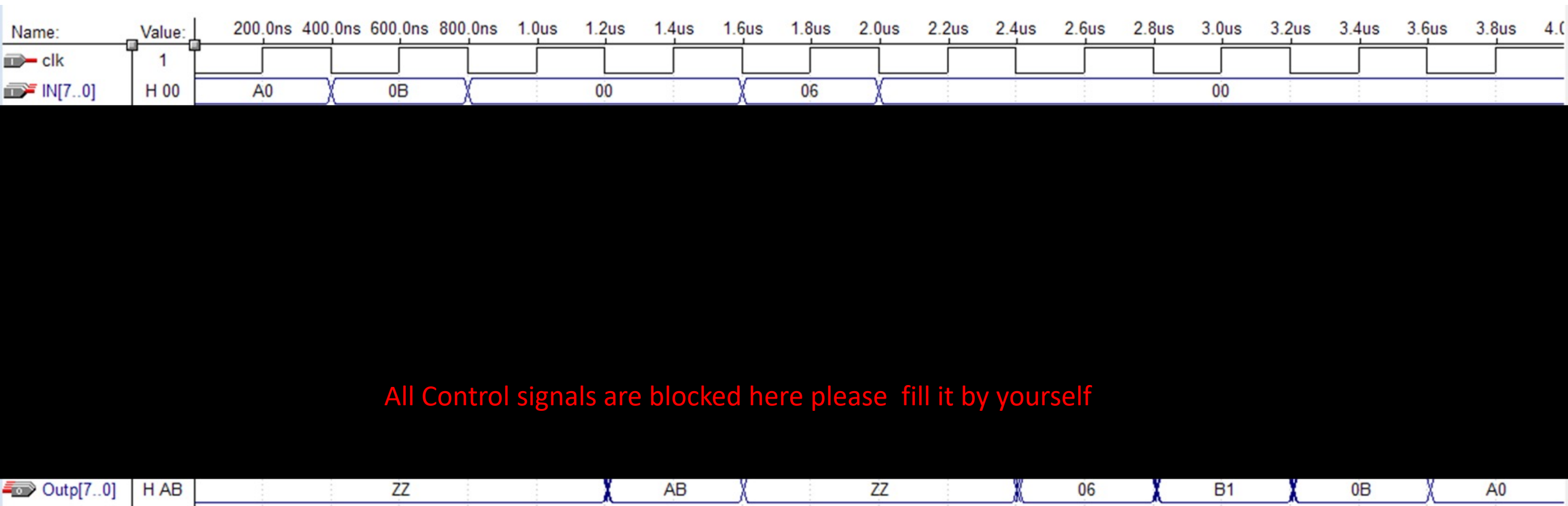

All Control signals are blocked here please fill it by yourself



Set End time to 4us.(File-> End Time)

Grid size to 200ns
(Options->Grid Size)


Possible Errors Part 1

- Your project may not be fit in device so you should do those steps:


- Select

- Assign

1. Devi

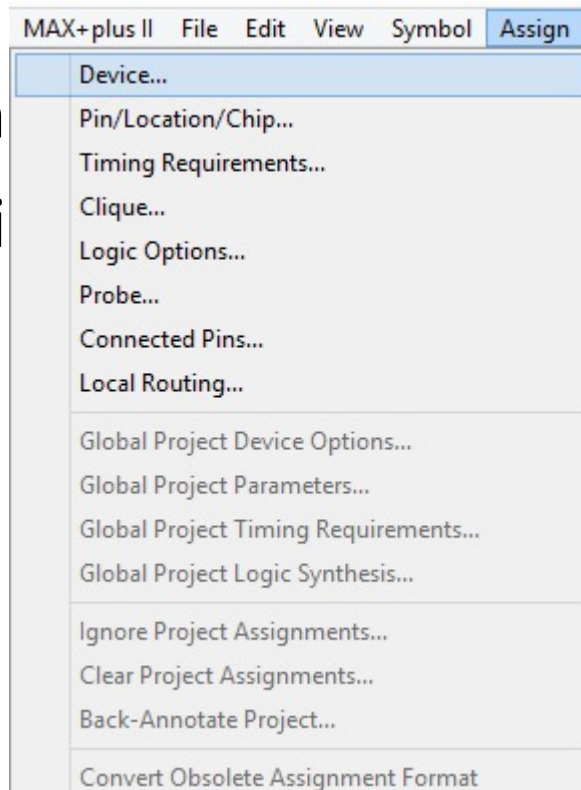

Select
Device Family
ACEX1K

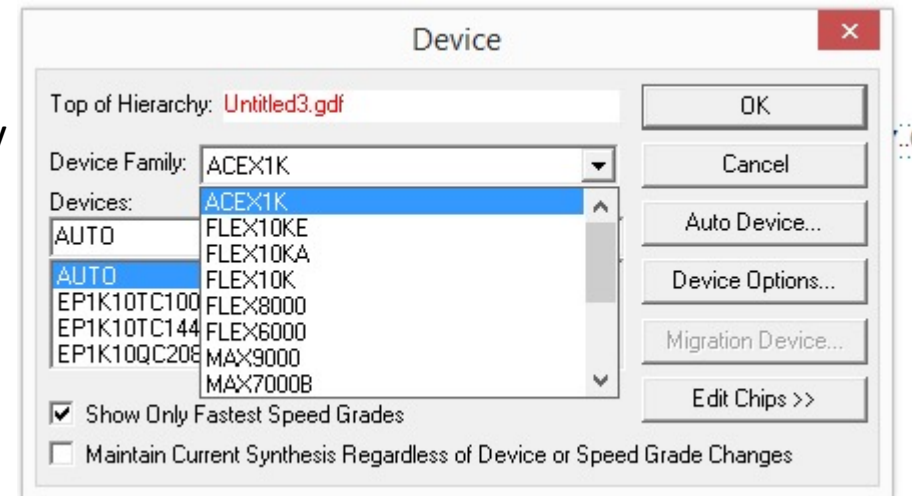


Possible Errors Part 2

- You may get an error like this




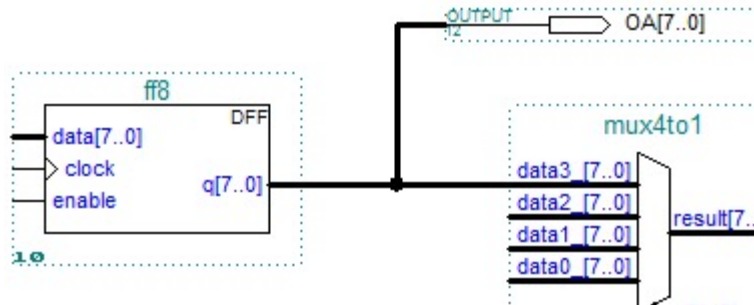- Please add 4 outputs for 4 flip flops. Ie:



Possible Errors Part 3

 If you put a 1 bit output for an 8 bit output it will give this error when you click save and check




Error: Width mismatch in pinstub "ff[3..0]" (ID ff[3..0]:4)

You have to change line to bold and write the necessary bit value to end of the output/signal




Hint 1 Adding a Component : 8 Bit Register: Part 1


1

 

2

 


3

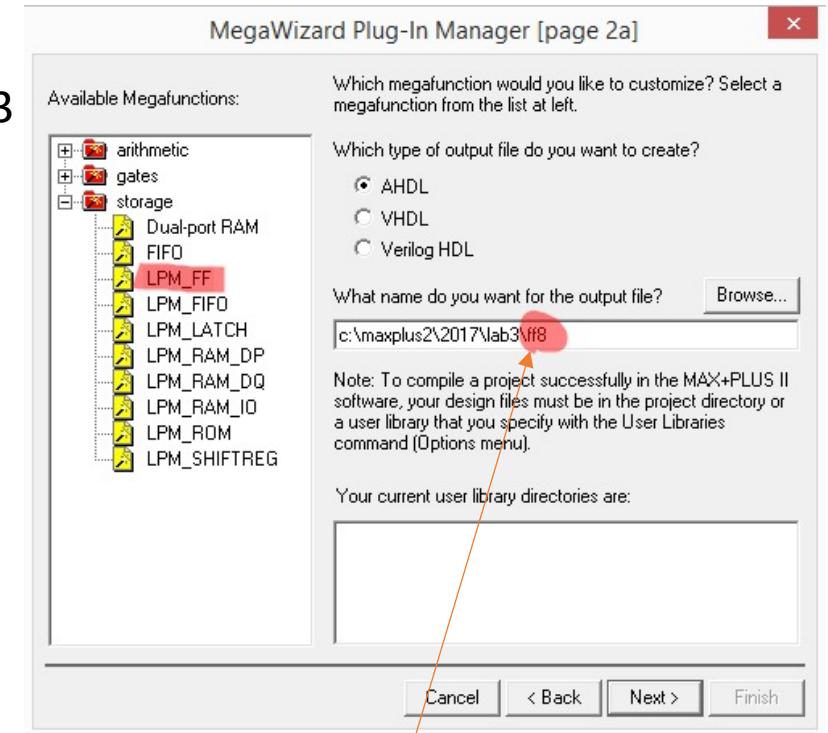

Please enter the path of your project file here

How to add 8 Bit Register: Part 2

4

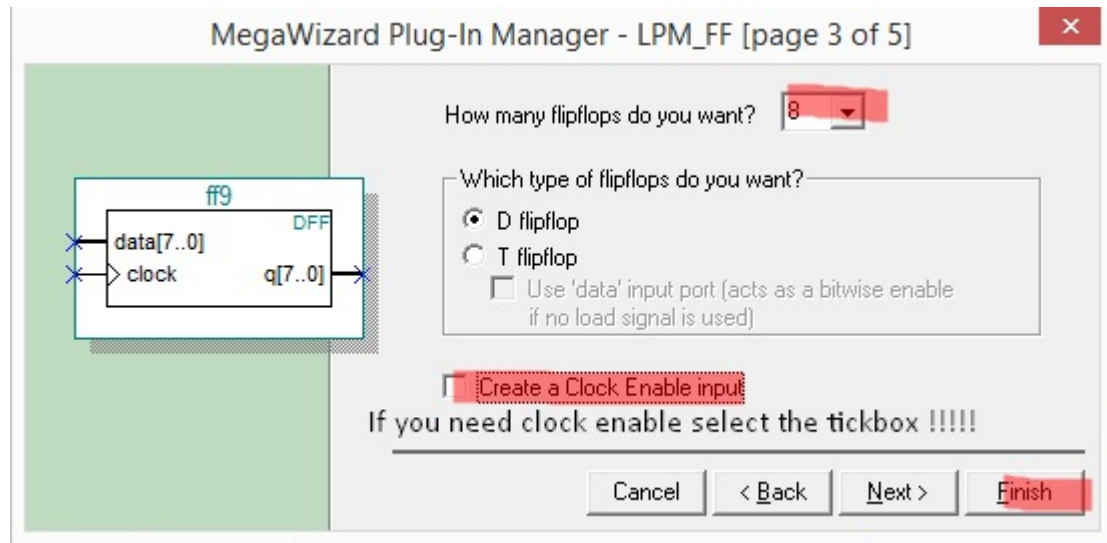


- Add the other necessary components. Please read all the options in component window Carefully

• !!!!!!!!!

Hint 2: Giving a value to signal simulation file


Part 1

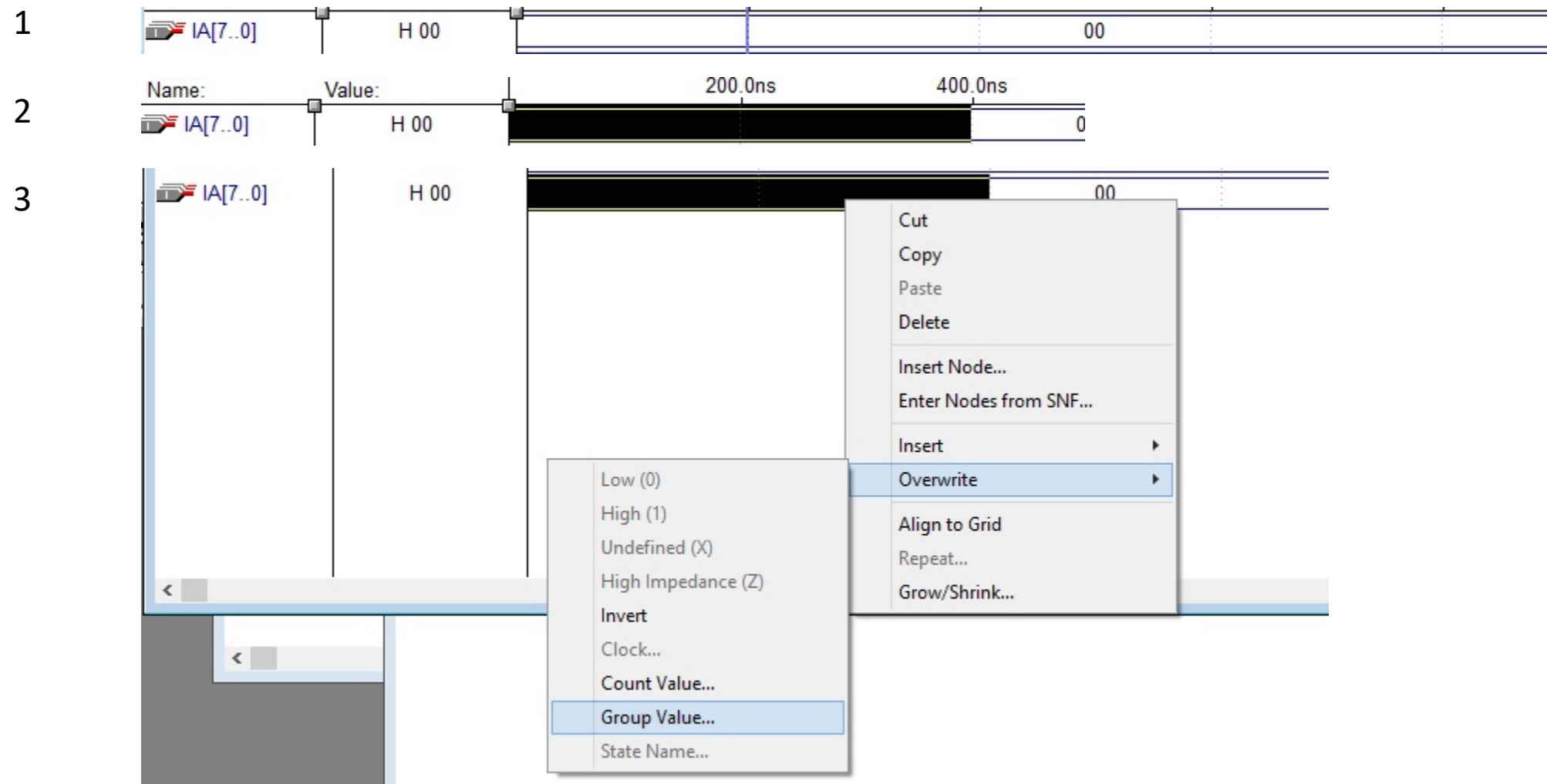

Hint 2: Giving a value to signal simulation file

Part 2

4

 

5

