
 


General Structure of a Microprocessor

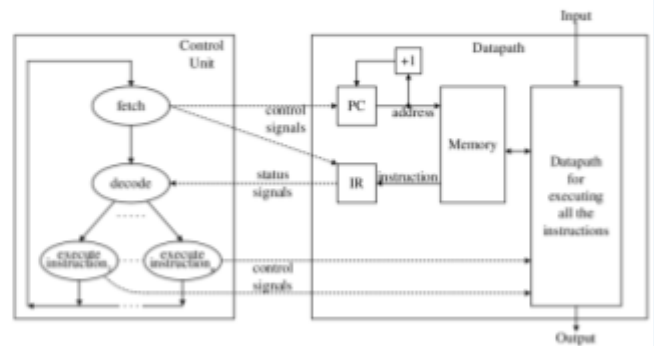

Overview of CPU Design



Datapath


Manipulates data. It includes:

- Functional units: Adder, shifter, multiplier, ALU (Arithmetic Logic Unit), comparator
- Registers and other memory elements for the temporary storage of the data
- Buses, multiplexers and tri-state buffers for the transfer of data between the different components in datapath and the external world.


Control yoksa, sadece inputlar geliyorsa ona datapath demiyoruz.

Why do we use datapath?

 - how do we design a circuit for performing more complex data operations or operations that involve multiple steps?



 
combinational circuit to add four numbers;




datapath to add one million numbers.

Designing Dedicated Datapaths:

$$A = A + 3$$

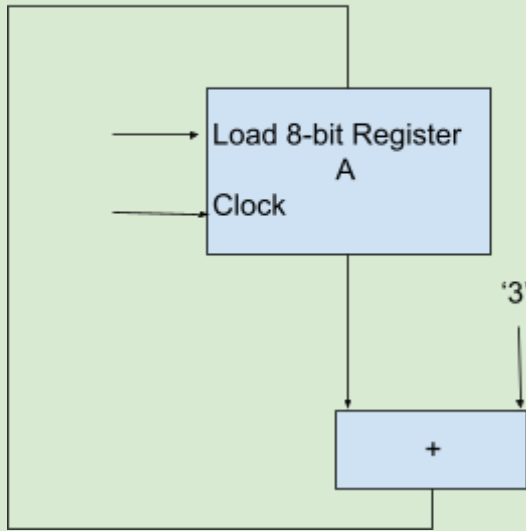

$$A = B + C$$

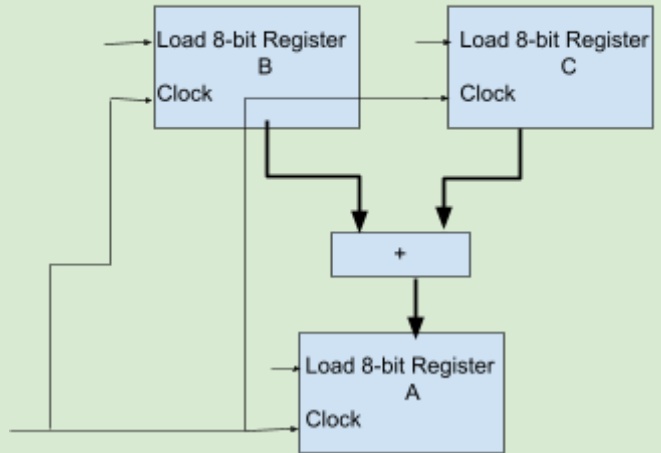

Multiplexers: Register'a göndereceğimiz **datayı seçmemizi sağlıyor**, min 2 inputlu oluyor 1 ve 0. Daha az adder Alu vs kullanmamızı sağlıyor.

Data Transfer: Multiple source olunca **multiplexer kullanarak data transfer etme olayı**, selection ile seçiyorsun hangi datayı transfer etmek istediğini.

Tri-State Bus: output gösterebilmek, bastırmak için kullanıyoruz. (**printf** gibi bişi aslında)


Generating Status Signals

Aslında olay condition(if statement gibi bir şey). Status signals are the results of the **conditional tests** that the datapath supplies to the control unit. *Caner anlatırken dersi or, and kapısı vs kullanmak yerine direkt adder "+" nasıl koyuyorsak "=" koyarak çizdi tahtaya. Sanırım sınavda da öyle yaparsak olur.*

Simple If-Then-Else

```
1      INPUT A
2      IF (A = 5) THEN
3          B = 8
4      ELSE
5          B = 13
6      END IF
7      OUTPUT B
```

Control Word	Instruction	ALoad	Muxsel	BLoad	Out
1	INPUT A	1	×	0	0
2	B = 8	0	1	1	0
3	B = 13	0	0	1	0
4	OUTPUT B	0	×	0	1

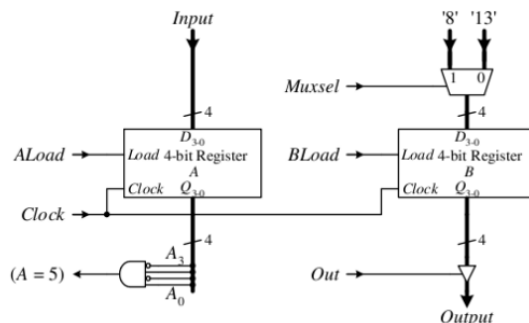


Example1

Counting 1 to 10


```

1      i = 0
2      WHILE (i ≠ 10) {
3          i = i + 1
4          OUTPUT i
5      }

```

 

Control Word	Instruction	$iLoad$	$Clear$	Out
1	$i = 0$	0	1	0
2	$i = i + 1$	1	0	0
3	OUTPUT i	0	0	1

 


Control Word	Instruction	$Count$	$Clear$	Out
1	$i = 0$	0	1	0
2	$i = i + 1$	1	0	0
3	OUTPUT i	0	0	1

Tabloya while'ın içindeki $i \neq 10$ u eklemiyoruz çünkü bir statement değil, sadece checkliyoruz orda.

while adding not operator($i \neq 10$ kısmı) to check whether it is equal or not, we dont need i selection column in the table cause we dont need a multiplexer.

VHDL for Datapath

Components of ALU

 

Right shift ->

01001100

00100110

Rotate --)

01001001

10100100

Register File


A register file is a means of **memory storage** within a computer's **central processing unit (CPU)**. The computer's register files **contain bits of data and mapping locations**. These locations specify certain addresses that are input components of a register file. Other inputs include data, a read and write function and execute function.

Factorial of n

```


1      INPUT  $n$ 
2       $product = 1$ 
3      WHILE ( $n > 1$ ) {
4           $product = product * n$ 
5           $n = n - 1$ 
6      }
7      OUTPUT  $product$ 

```

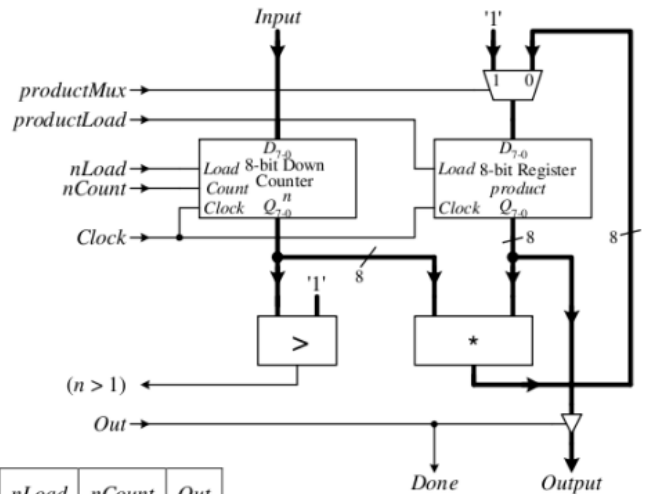

Control Word	Instruction	$productMux$	$productLoad$	$nLoad$	$nCount$	Out
1	INPUT n	\times	0	1	0	0
2	$product = 1$	1	1	0	0	0
3	$product = product * n$	0	1	0	0	0
4	$n = n - 1$	\times	0	0	1	0
5	OUTPUT $product$	\times	0	0	0	1

Control Word	Instruction	$productMux$	$productLoad$	$nLoad$	$nCount$	Out
1	INPUT $n, product = 1$	1	1	1	0	0
2	$product = product * n, n = n - 1$	0	1	0	1	0
3	OUTPUT $product$	\times	0	0	0	1

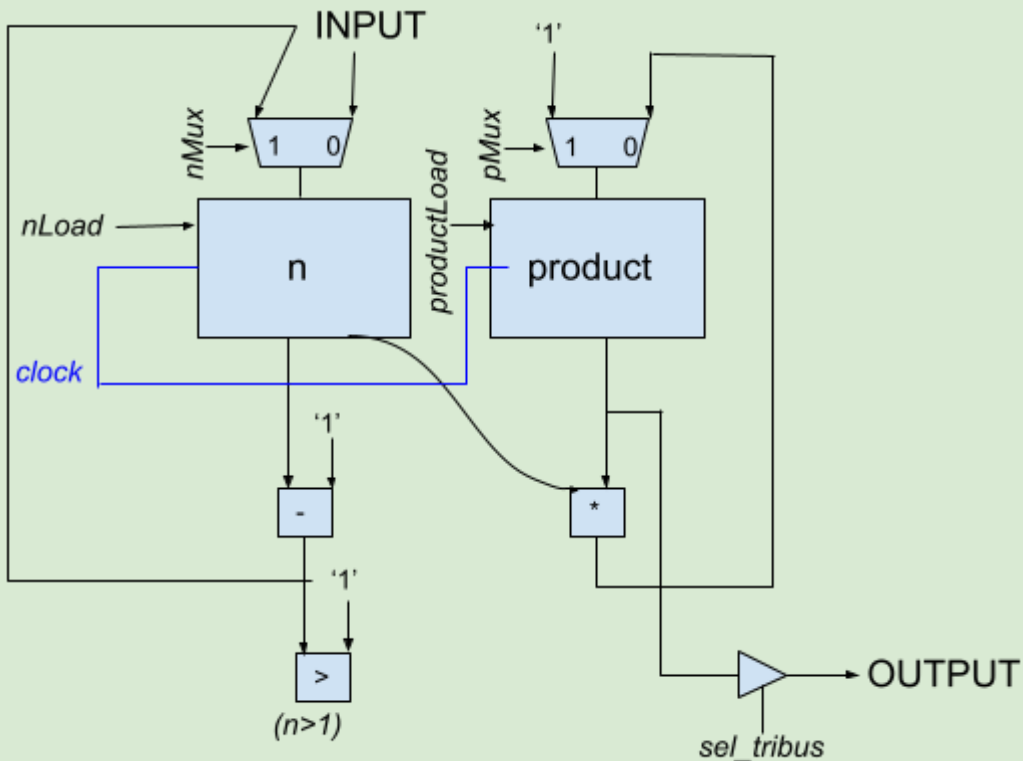

General Purpose Databath

```


1      sum = 0
2      INPUT n
3      WHILE (n ≠ 0){
4          sum = sum + n
5          n = n - 1
6      }
7      OUTPUT sum

```

ALU_2	ALU_1	ALU_0	Operation
0	0	0	Pass through A
0	0	1	A AND B
0	1	0	A OR B
0	1	1	NOT A
1	0	0	$A + B$
1	0	1	$A - B$
1	1	0	$A + 1$
1	1	1	$A - 1$

SH_1	SH_0	Operation
0	0	Pass through
0	1	Shift left and fill with 0
1	0	Shift right and fill with 0
1	1	Rotate right

Control Word	Instruction	IE 15	WE 14	$WA_{1,0}$ 13-12	RAE 11	$RAA_{1,0}$ 10-9	RBE 8	$RBA_{1,0}$ 7-6	$ALU_{2,1,0}$ 5-3	$SH_{1,0}$ 2-1	OE 0
1	$sum = 0$	0	1	00	1	00	1	00	101 (subtract)	00	0
2	INPUT n	1	1	01	0	xx	0	xx	xxx	xx	0
3	$sum = sum + n$	0	1	00	1	00	1	01	100 (add)	00	0
4	$n = n - 1$	0	1	01	1	01	0	xx	111 (decrement)	00	0
5	OUTPUT sum	x	0	xx	1	00	0	xx	000 (pass)	00	1

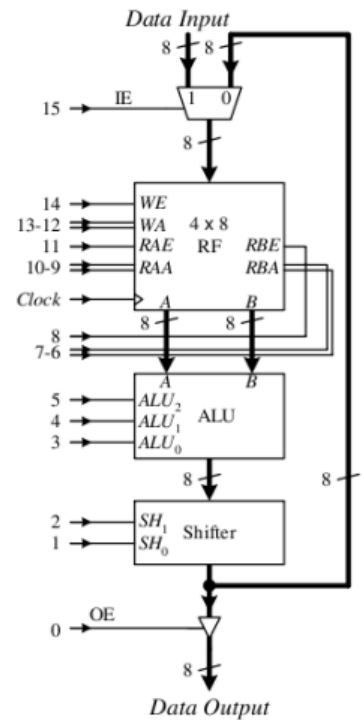

Example: Write the control words for manipulating the above circuit to perform the following program

Multiplication of two unsigned numbers:

```

1      prod = 0
2      INPUT A
3      INPUT B
4      WHILE (B ≠ 0){
5          prod = prod + A
6          B = B - 1
7      }
8      OUTPUT prod
    
```

Control Word	Instruction	IE 15	WE 14	WA _{1,0} 13-12	RAE 11	RAA _{1,0} 10-9	RBE 8	RBA _{1,0} 7-6	ALU _{2,1,0} 5-3	SH _{1,0} 2-1	OE 0
1	<i>prod</i> = 0	0	1	00	1	00	1	00	101 (subtract)	00	0
2	INPUT A	1	1	01	0	xx	0	xx	xxx	xx	0
3	INPUT B	1	1	10	0	xx	0	xx	xxx	xx	0
4	<i>prod</i> = <i>prod</i> + A	0	1	00	1	00	1	01	100 (add)	00	0
5	<i>B</i> = <i>B</i> - 1	0	1	10	1	10	0	xx	111 (decrement)	00	0
6	OUTPUT <i>prod</i>	x	0	xx	1	00	0	xx	000 (pass)	00	1